

Radio Frequency counter

Written by Hans Summers

Saturday, 05 September 2009 22:45 - Last Updated Saturday, 05 September 2009 22:52



This very tiny frequency counter was built to fit inside the front panel of a radio transceiver. It now occupies pride of place in the front panel of my [HF Receiver](#), alongside my panel mounting clock. One of the switches is used to switch the counter on and off, the other sets the display resolution. The two choices for display resolution are 1Hz, which will read one measurement per second, or 10Hz, which will read 10 measurements per second. The decimal points are automatically displayed in the correct position to indicate MHz and KHz markers. The counter uses CMOS 74HC chips. Like the matching clock, the counter uses switching of the display LEDs instead of a real voltage regulator. Unlike the clock, it didn't undergo a meltdown...

{gallery}radiofreqcounter/photos{/gallery}

The counter is shown in the photo above with the matching panel mounting clock in the background, measuring a frequency of 384 KHz from the timing chain of the clock.

The counter is encased in single-sided unetched PCB material, soldered together on the inside into a box shape. The nuts on the toggle switches are used to secure the counter inside the case of a radio transceiver. I actually built this counter during my finals at university, it was a good break.

At the left of the counter a coil can be seen - this is input filtering of the supply voltage, the idea being to prevent spurious signals from the frequency counter's timing chain from entering the host radio receiver.

The circuit is built on a triple-decker vero-board arrangement (see right). Compact, but difficult

Radio Frequency counter

Written by Hans Summers

Saturday, 05 September 2009 22:45 - Last Updated Saturday, 05 September 2009 22:52

to make repairs! On the left note the coil for supply line filtering. The bolts protruding from the rear circuit board are used to fix the assembly in it's PCB-material case, although its such a tight fit they're scarcely needed!

Circuit Diagrams (schematics)

[CLICK HERE](#) for an Adobe Acrobat .pdf file containing the three pages of circuit diagrams.

Page 1: Counting chain, display decoders and 7-segment displays.

Page 2: Timing chain and logic.

Page 3: The placement of the chips on the boards, and pinouts.

Errata

Thanks to Jonathan Kelly MW3KGQ who pointed out that the 4-bit ABCD inputs to the 4511 chips are incorrect on the bottom four 4511 chips on the page. The correct order for A B C D is pins 7 1 2 6 for ALL EIGHT chips, as in the top few on the diagram. Thanks Jonathan, well spotted!