

[Introduction](#)

[Spectrum Analyser theory](#)

[Construction Techniques](#)

**Power Supply**

[Sweep Generator](#)

[Logarithmic Amplifier](#)

[145 MHz IF Filter](#)

[1st Mixer](#)

[2nd Mixer](#)

[8 MHz IF Filter](#)

[Low-pass Filter](#)

[Input Attenuator](#)

[10MHz Crystal Calibrator](#)

[Alignment and Operation](#)

## The simple man's Spectrum Analyser Power Supply

{gallery}sapsu/1{/gallery}

The first thing to build is the power supply, obviously a prerequisite for operating any of the other modules. This PSU supplies regulated voltages of +12V, +6V, +5V and -5V. The design is fairly standard, using 78xx-series regulators. The transformer has two 15V secondaries rated 250mA each. I bolted the regulators to a piece of single-sided PCB stock which is in turn bolted to the back wall of the case. Holes drilled in the back wall provide a degree of ventilation.

{gallery}sapsu/2{/gallery}

## Alternative circuit

